

Mach3 Pin Utilization:

P1 - from cpu - Heartbeat
P2 - from cpu - X Pulse
P3 - from cpu - X Dir
P4 - from cpu - Y Pulse
P5 - from cpu - Y Dir
P6 - from cpu - Z Pulse
P7 - from cpu - Z Dir
P10 - to cpu - Estop
P12 - to cpu - Handwheel A
P13 - to cpu - Handwheel B
P14 - from cpu - Spindle On
P16 - from cpu - Aux1 On
P17 - from cpu - Aux2 On

Notes:


1. System uses a commercial UC100 USB to 25 pin parallel port adapter.
2. Signals are carried from the UC100 parallel side to the main board through a commercial DB25 1205 opto-isolated breakout board.

Relays:

RLA - 5v. - Software OK
RLB - 24v. - Interface OK
RLC - 5v. - Servo Enable
RLD - 5v. - Spindle on Cmd.
RLE - 24v. - Spindle Power
RLF - 5v. - Aux1 on Cmd.
RLG - 5v. - Aux2 on Cmd.
RLH - 24v. - Aux1 Power

Notes:

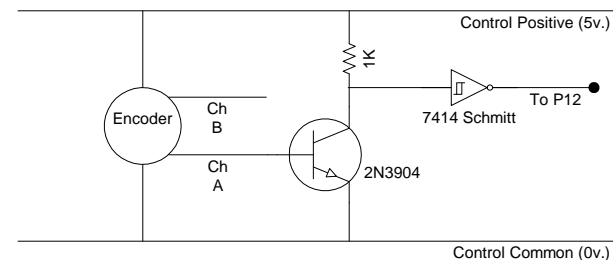
1. RLA is a commercial charge pump board designed to respond to Mach3's heartbeat signal.
2. Relays RLC, RLD, RLF and RLG are located on an opto-isolated commercial board which accepts 5v. TTL inputs.
3. The 24v. relays are 'ice cube' style on DIN-rail.



Pendant Encoder Signal Conditioning Circuit

Notes:



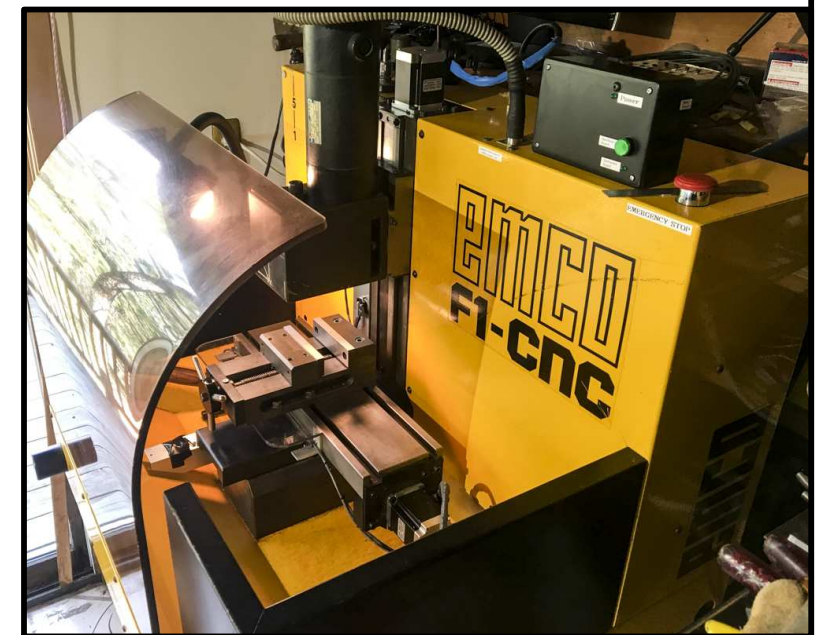
1. Circuit shown for channel A, only. Both channels are identical.
2. Circuit is packaged within pendant.



Emco F1 Mill Stepper Upgrade

Safety and Control Logic Diagram

9/12/17 - Mark McDade - P1 of 2

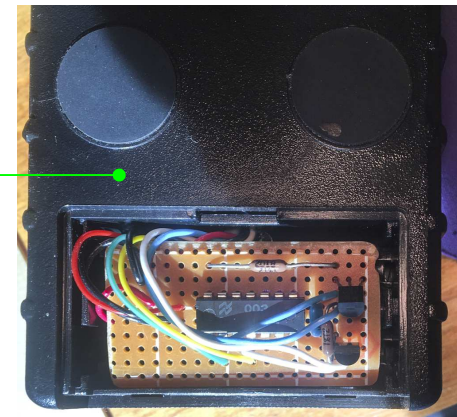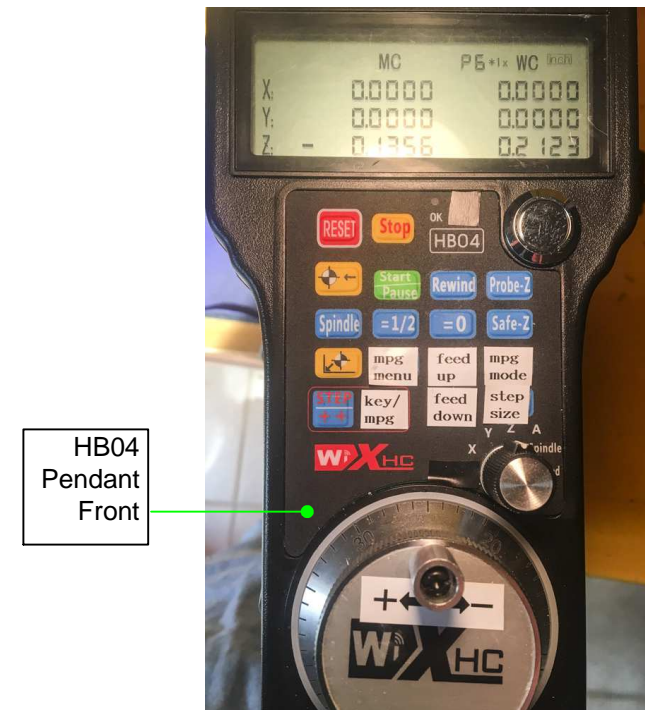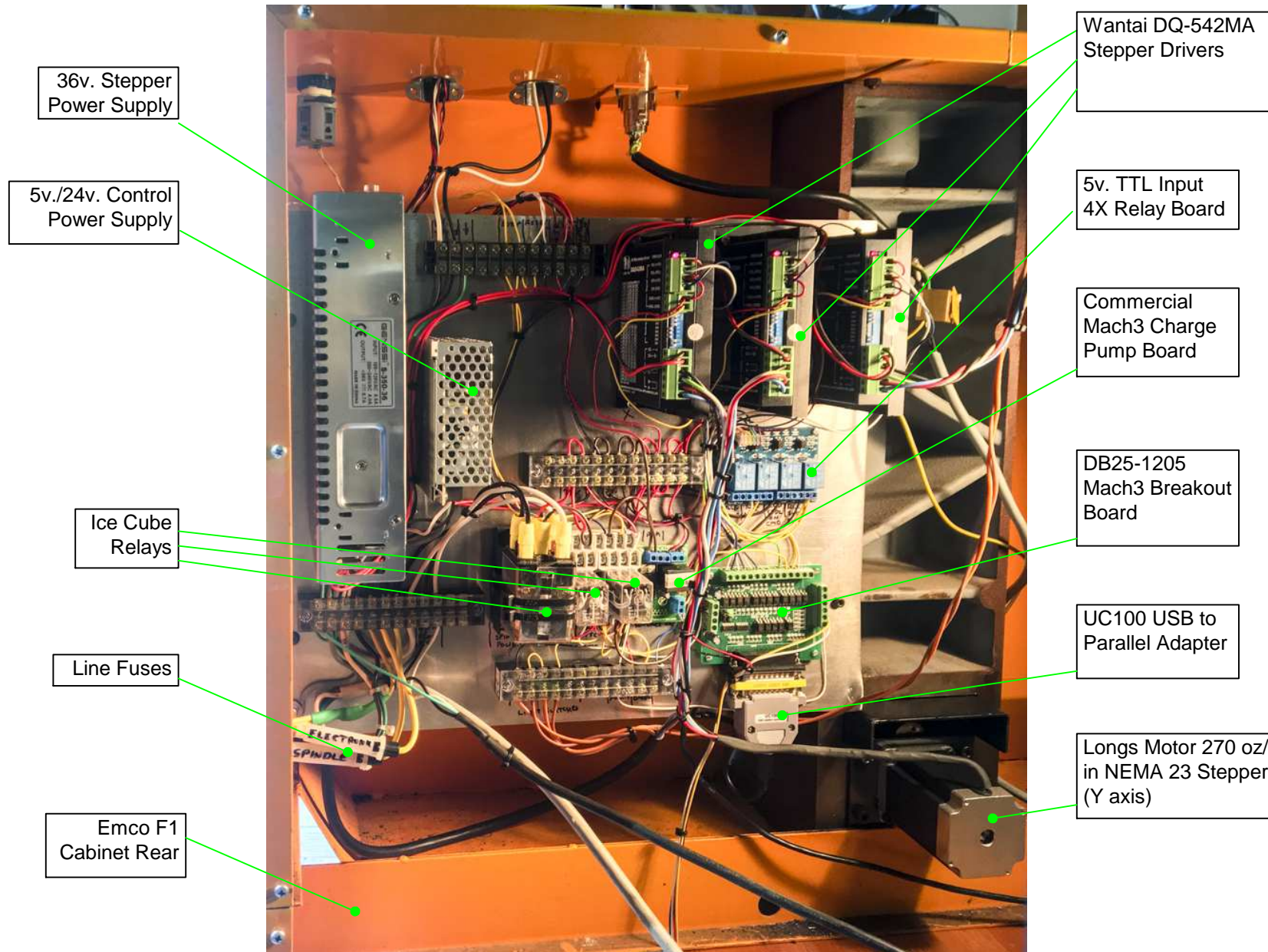

Emco F1 Mill Stepper Upgrade

Safety and Control Circuit Layout

9/12/17 - Mark McDade - P2 of 2